

Combinational Logic Design using ROM Array

Read-Only Memory (ROM)

- Combinational circuits are often referred to as **memoryless** circuits, because their output depends only on their current input and no history of prior inputs is retained.
- There is a type of memory that is implemented with combinational circuits, namely **read-only memory (ROM)**.


Read-Only Memory (ROM)

- ROM is a memory unit that performs only the read operation
- Binary information stored in a ROM is permanent and is created during the fabrication process
- A given input to the ROM (address lines) always produces the same output (data lines)
- Because the outputs are a function only of the present inputs, ROM is a combinational circuit

- ROM is a **programmable logic device** (PLD). The binary information that is stored within such a device is specified in some fashion and then embedded within the hardware in a process is referred to as programming the device.
- Other such units of PLD are the **programmable logic array** (PLA), **programmable array logic** (PAL), and the **field-programmable gate array** (FPGA).

- A **word** is the basic unit that moves in and out of memory
- The length of a word is often multiples of a byte (=8 bits)
- Memory units are specified by its **number of words** and the **number of bits** in each word

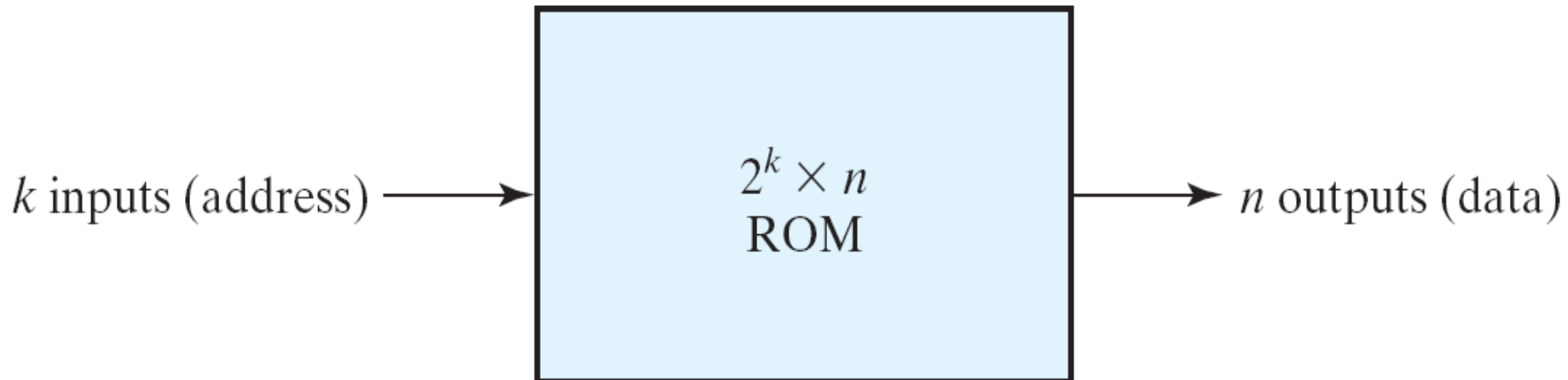- A ROM is essentially a memory device in which permanent binary information is stored



- Ex: 1024(words) x 16(bits)
 - Each word is assigned a particular **address**, starting from 0 up to $2^k - 1$ (k = number of address lines)

Read-Only Memory (ROM)

- A ROM can be implemented with a decoder and a set of OR gates.

For a $2^k \times n$ ROM,
it consists of

- k inputs (address line) and n outputs (data)
- 2^k words of n -bit each
- A $k \times 2^k$ decoder (generate all minterms)
- n OR gates with 2^k inputs
- Initially, all inputs of OR gates and all outputs of the decoder are fully connected


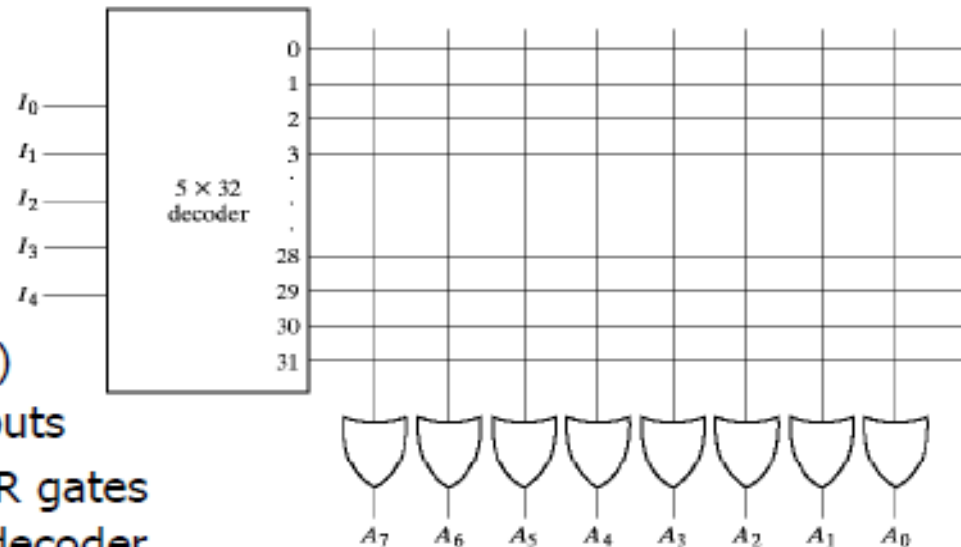


Fig. 7-10 Internal Logic of a 32 x 8 ROM


Programming the ROM

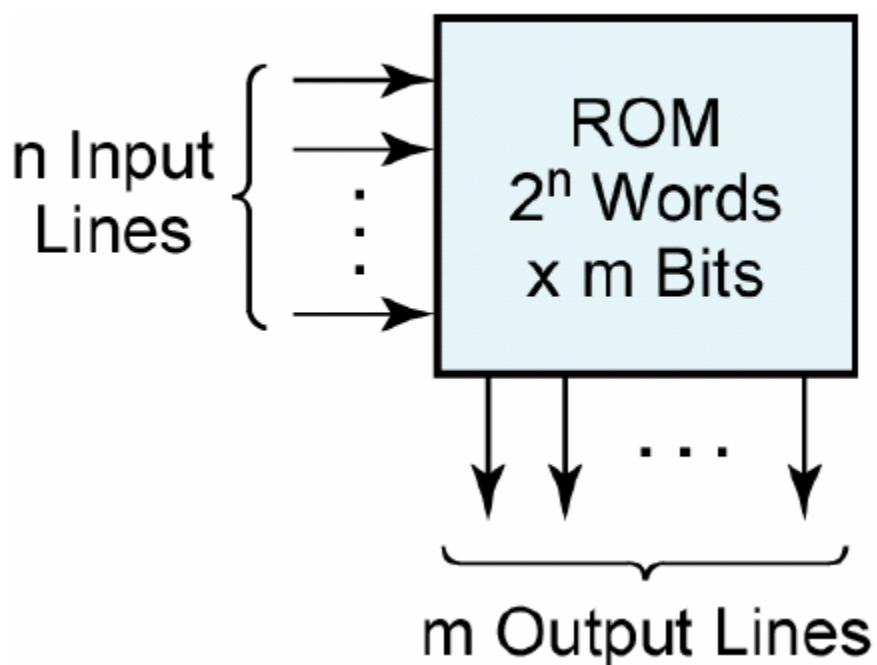- Each intersection (crosspoint) in the ROM is often implemented with a fuse.
- Blow out unnecessary connections according to the truth table
 - 1 means connected (marked as X)
 - 0 means unconnected
- Cannot recovered after programmed




n Input Variables	m Output Variables
00 . . . 00	100 . . . 110
00 . . . 01	010 . . . 111
00 . . . 10	101 . . . 101
00 . . . 11	110 . . . 010
⋮	⋮
11 . . . 00	001 . . . 011
11 . . . 01	110 . . . 110
11 . . . 10	011 . . . 000
11 . . . 11	111 . . . 101

ROM Structure

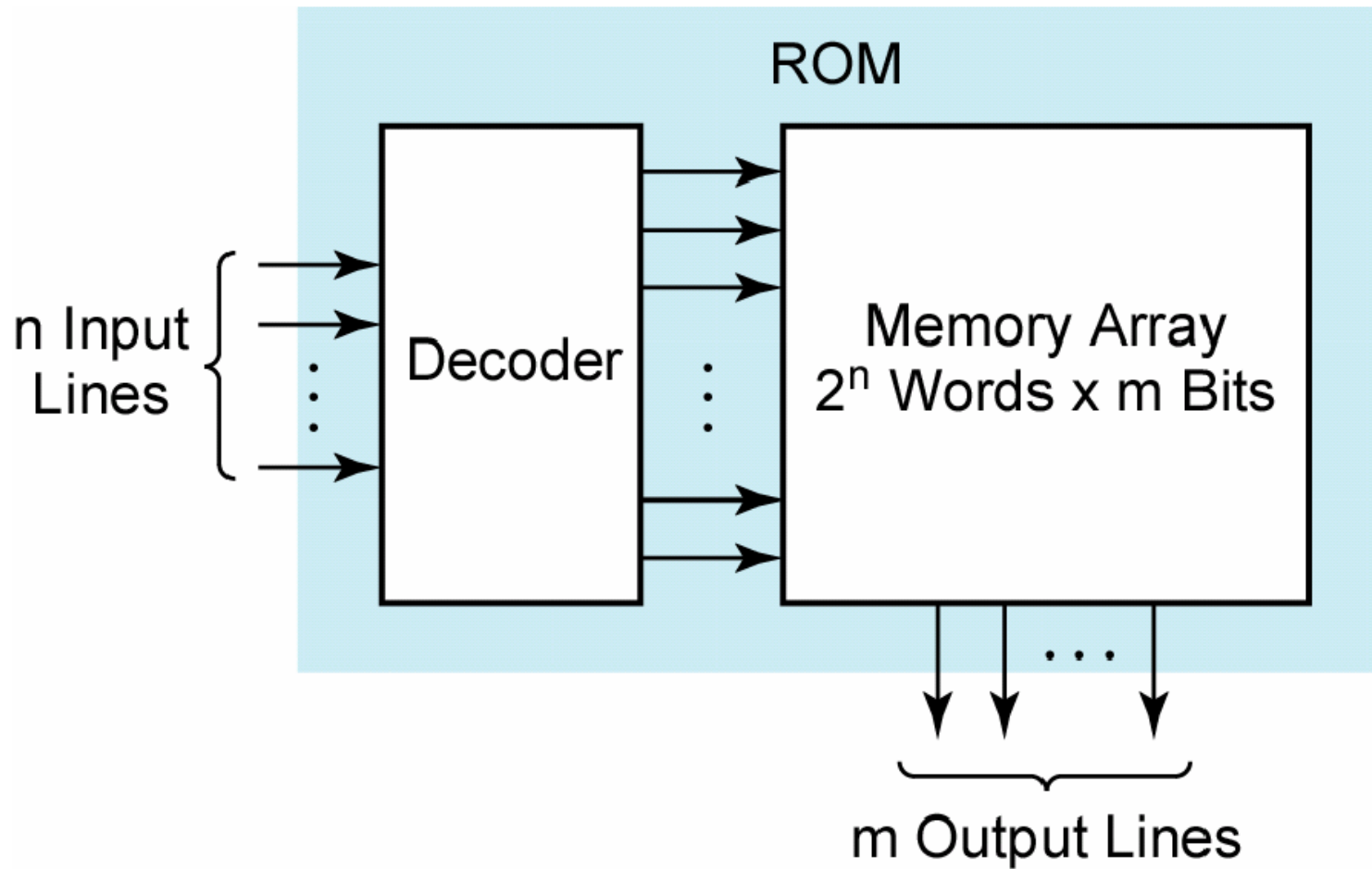


Example


3 Inputs
Lines

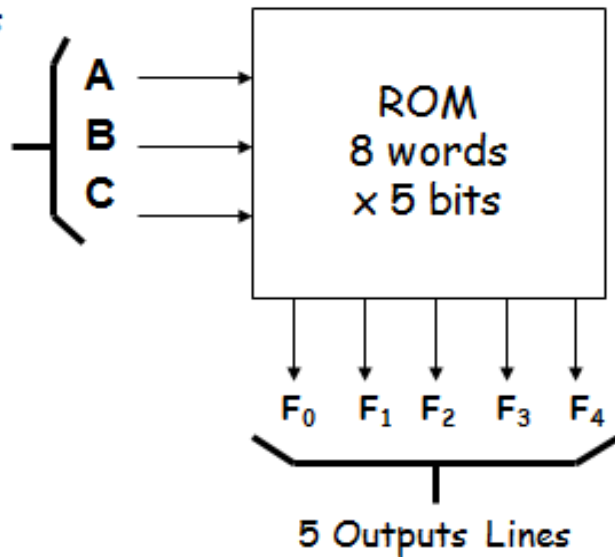

A	B	C	F ₀	F ₁	F ₂	F ₃	F ₄
0	0	0	0	1	0	1	0
0	0	1	1	1	1	1	0
0	1	0	0	0	0	1	1
0	1	1	1	1	1	0	1
1	0	0	0	1	0	1	0
1	0	1	0	1	1	1	1
1	1	0	1	0	1	0	1
1	1	1	1	1	0	1	0

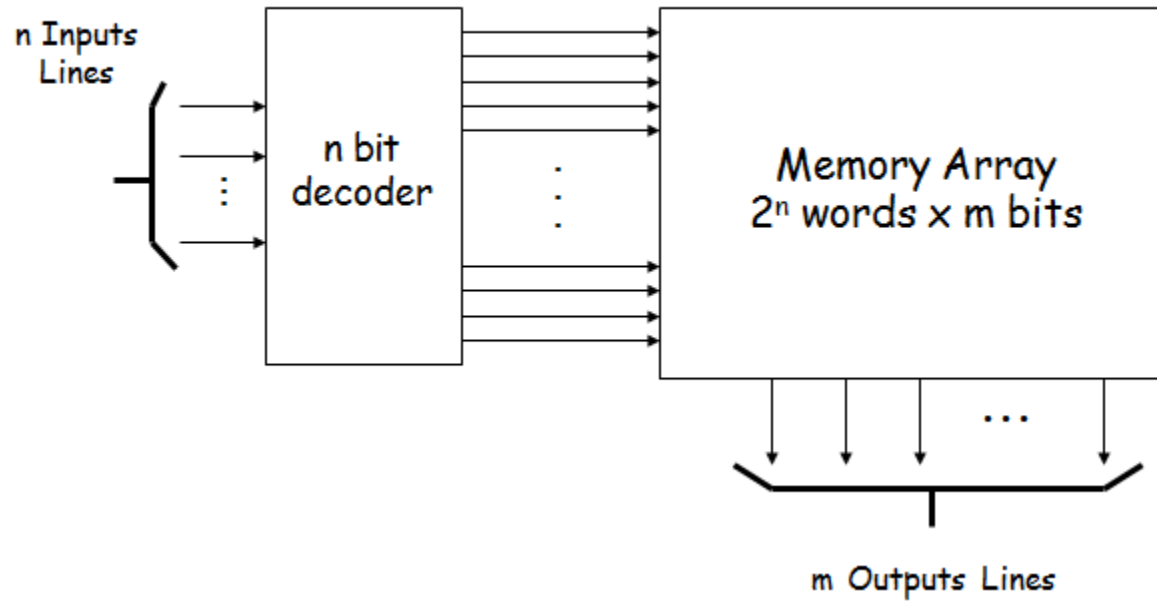


ROM Memory Array

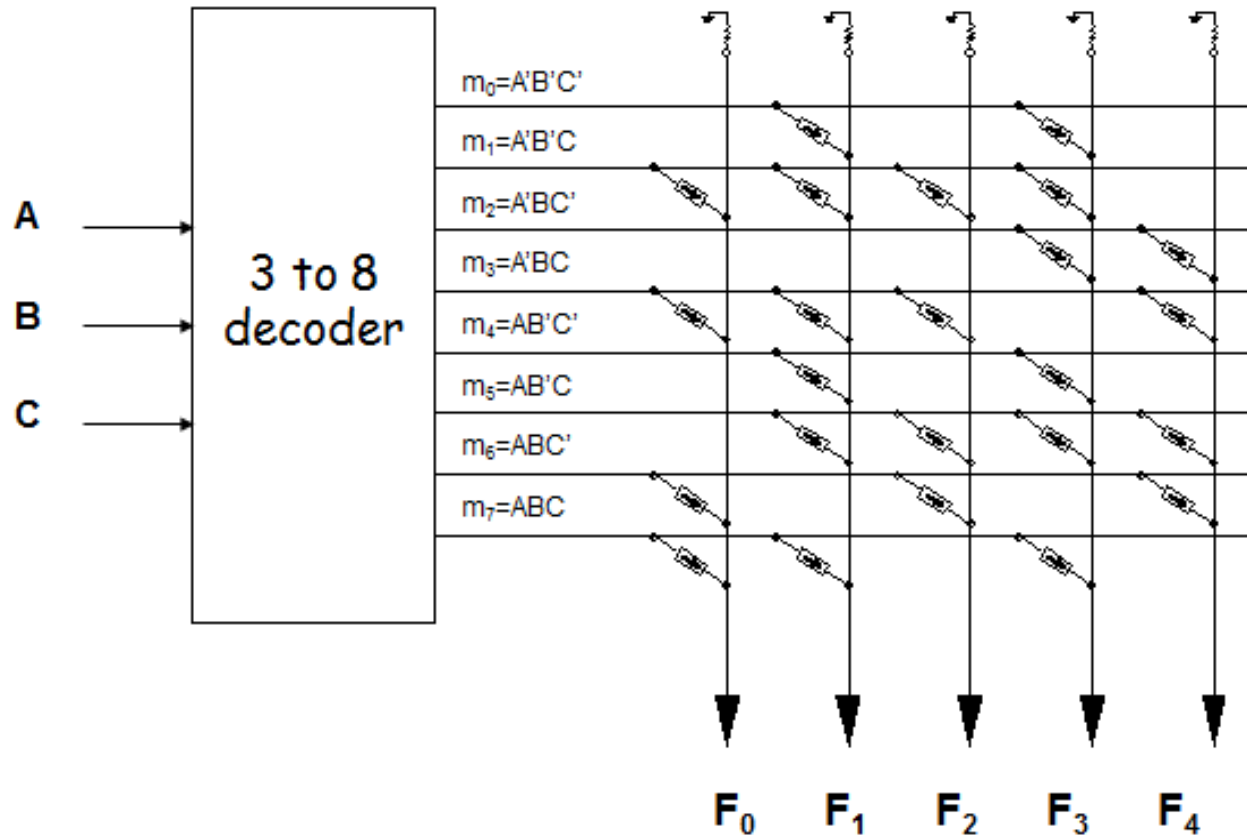

ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		\vdots						\vdots				
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

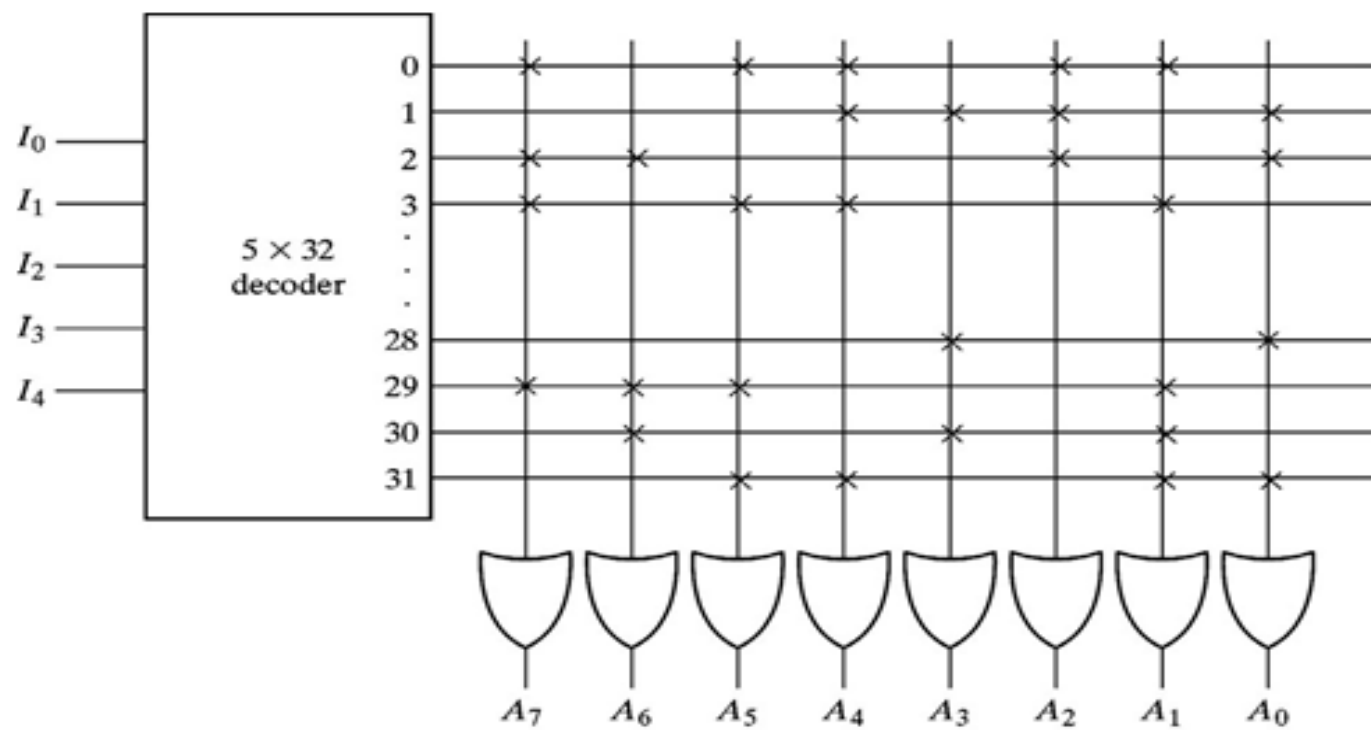


Design Comb. Circuit with ROM

- Derive the truth table of the circuit
- Determine minimum size of ROM
- Program the ROM

- Design a combinational circuit using a ROM. The circuit accepts a three-bit number and outputs a binary number equal to the square of the input number.

Example

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

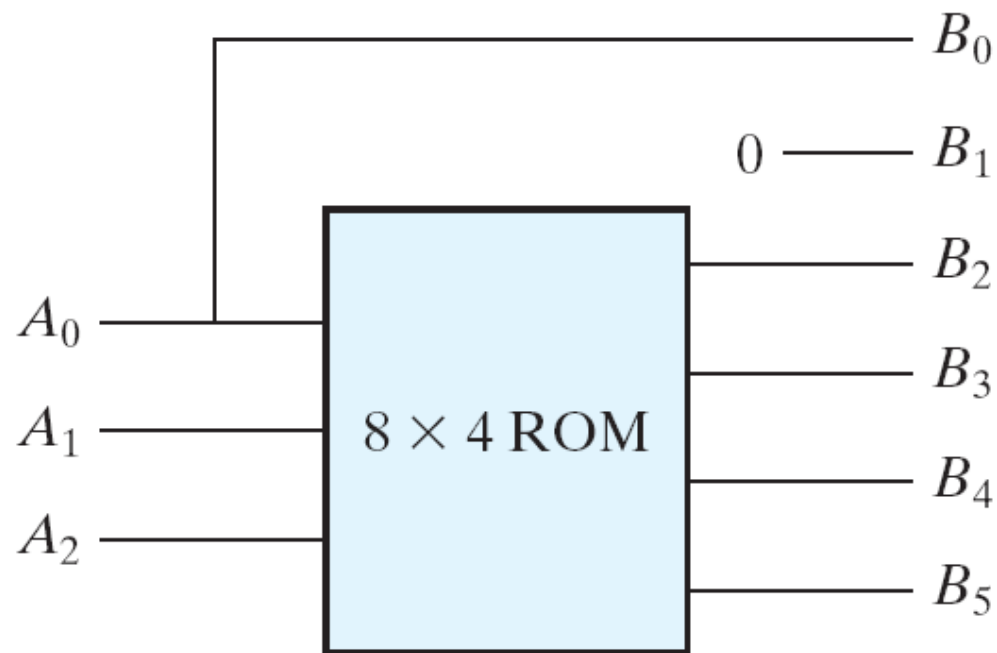

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

