

Application of Flip flops

Application of Flip flops

- Registers
- Counters
- Shift registers

Registers

- A register is a memory device that can be used to store more than one bit of information.
- A register is usually realized as several flip-flops with common control signals that control the movement of data to and from the register.

- Common refers to the property that the control signals apply to all flip-flops in the same way
- A register is a generalization of a flip-flop.
- A flip flop stores one bit, a register stores several bits
- The main operations on a register are the same as for any storage devices, namely
 - Load or Store: Put new data into the register
 - Read: Retrieve the data stored in the register (usually without changing the stored data)

Counters

- Counters are a specific type of sequential circuit or registers.
- Counters are sequential circuits which "count" through a specific state sequence. They can count up, count down, or count through other fixed sequences.

Shift Registers

- They are used for storage and transfer of data.
- Shift registers have no specific sequence of states unlike counters.

Benefits of counters

- Counters can act as simple clocks to keep track of time.
 - How many bits have been sent or received?
 - How many steps have been performed in some computation?
- All processors contain a **program counter**, or **PC**.
 - Programs consist of a list of instructions that are to be executed one after another (for the most part).
 - The PC keeps track of the instruction currently being executed.
 - The PC increments once on each clock cycle, and the next program instruction is then executed.

- Counters are important components in computers
 - The increment or decrement by one in response to input
- A counter that follows the binary number sequence is called a binary counter
 - n-bit binary counter: n flip-flops, count in binary from 0 to 2^n-1

Modulus

- Each of the counts of the counter is called **state** of the counter.
- A counter with n flip-flops can have 2^n states and of same modulus.
- The number of states in a counter is known as its mod (modulo) number.
- Thus a 2-bit counter is a mod-4 counter.
- A mod- n counter may also be described as a divide-by- n counter.

- Counter is a Clocked sequential circuit whose state diagram contains a single cycle.
- The number of flip-flops determines the count limit or number of states.
- For example, a Modulus-12 counter would count from 0 (0000) to 11 (1011) and requires four flip-flops (16 states - 12 used).

- Counters with non-power of 2 modulus has unused states

Types of counter

- Counters are available in two types
 - Synchronous Counters(parallel counters)
 - Asynchronous Counters (Ripple Counters)

- **Synchronous Counters:**
 - A common clock signal is connected to the C input of each flip-flop
- **Ripple Counters**
 - Clock connected to the flip-flop clock input on the LSB bit flip-flop
 - For all other bits, a flip-flop output is connected to the clock input, thus circuit is not truly synchronous
 - Output change is delayed more for each bit toward the MSB.

- Ripple counter let some flip-flop output to be used as clock signal source for other flip-flop
- Synchronous counter use the same clock signal for all flip-flop
 - Synchronous counters are faster than asynchronous counters because of the simultaneous clocking.
 - Synchronous counters are an example of *state machine* design because they have a set of states and a set of transition rules for moving between those states after each clocked event.


Other Counters

- **Binary counter**
 - Counter that follows a binary sequence
 - N bit binary counter counts in binary from 0 to $2^n - 1$
- **Down Counter** - counts downward instead of upward
- **Up-Down Counter** - counts up or down depending on value a control input such as Up/Down
- **Parallel Load Counter** - Has parallel load of values available depending on control input such as Load

- Divide-by-n (Modulo n) Counter
- Count is remainder of division by n; n may not be a power of 2
- Count is arbitrary sequence of n states specifically designed state-by-state
- Includes modulo 10 which is the BCD counter


Two-bit asynchronous counter

 Output from one flip-flop is connected to clock input for the next flip-flop MSB




00 → 01 → 10 → 11 → 00

3-bit ripple/asynchronous counter

 


Asynchronous Down Counter

 - Down asynchronous counter count from large to zero and repeat
- Example: 3-bit binary down counter



3-bit binary
up counter

 


3-bit binary
down counter

Synchronous Counter (Parallel)

- Synchronous counter: flip-flop with the same synchronous clock signal
- We can build synchronous counter using process to design sequential circuit
- Example: 2-bit synchronous binary counter (using T flip-flop or JK)

 - Example: 2-bit synchronous binary counter (using T flip-flop or JK)




Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1'	A_0'	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = \mathcal{A}_0$$


$$TA_0 = 1$$

- Example: 3-bit synchronous binary counter (using T flip)


Present state			Next state			Flip-flop inputs		
A_2	A_1	A_0	A_2^+	A_1^+	A_0^+	TA_2	TA_1	TA_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

 

$$TA_2 = A_1 \cdot A_0$$

 


$$TA_1 = A_0$$

 

$$TA_0 = 1$$

Designing Synchronous Counter

 - Example: 3-bit Gray Code Counter (using JK flip-flop)



Present state			Next state			Flip-flop inputs					
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	JQ_2	KQ_2	JQ_1	KQ_1	JQ_0	KQ_0
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	1	0	X	1	X	X	0
0	1	0	1	1	0	1	X	X	0	0	X
0	1	1	0	1	0	0	X	X	0	X	1
1	0	0	0	0	0	X	1	0	X	0	X
1	0	1	1	0	0	X	0	0	X	X	1
1	1	0	1	1	1	X	0	X	0	1	X
1	1	1	1	0	1	X	0	X	1	X	0

		Q_1Q_0			
		00	01	11	10
Q_2	0				1
	1	X	X	X	X

$JQ_2 = Q_1 \cdot Q_0'$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X	X	X	X
	1	1			

$KQ_2 = Q_1' \cdot Q_0'$

		Q_1Q_0			
		00	01	11	10
Q_2	0		1	X	X
	1			X	X

$JQ_1 = Q_2' \cdot Q_0$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X	X		
	1	X	X	1	

$KQ_1 = Q_2 \cdot Q_0$


		Q_1Q_0			
		00	01	11	10
Q_2	0	1	X	X	
	1		X	X	1

$JQ_0 = Q_2 \cdot Q_1 + Q_2' \cdot Q_1'$
 $= (Q_2 \oplus Q_1)'$

		Q_1Q_0			
		00	01	11	10
Q_2	0	X		1	X
	1	X	1		X

$KQ_0 = Q_2 \cdot Q_1' + Q_2' \cdot Q_1$
 $= Q_2 \oplus Q_1$

$$\begin{array}{lll}
 JQ_2 = Q_1 \cdot Q_0' & JQ_1 = Q_2' \cdot Q_0 & JQ_0 = (Q_2 \oplus Q_1)' \\
 KQ_2 = Q_1' \cdot Q_0' & KQ_1 = Q_2 \cdot Q_0 & KQ_0 = Q_2 \oplus Q_1
 \end{array}$$

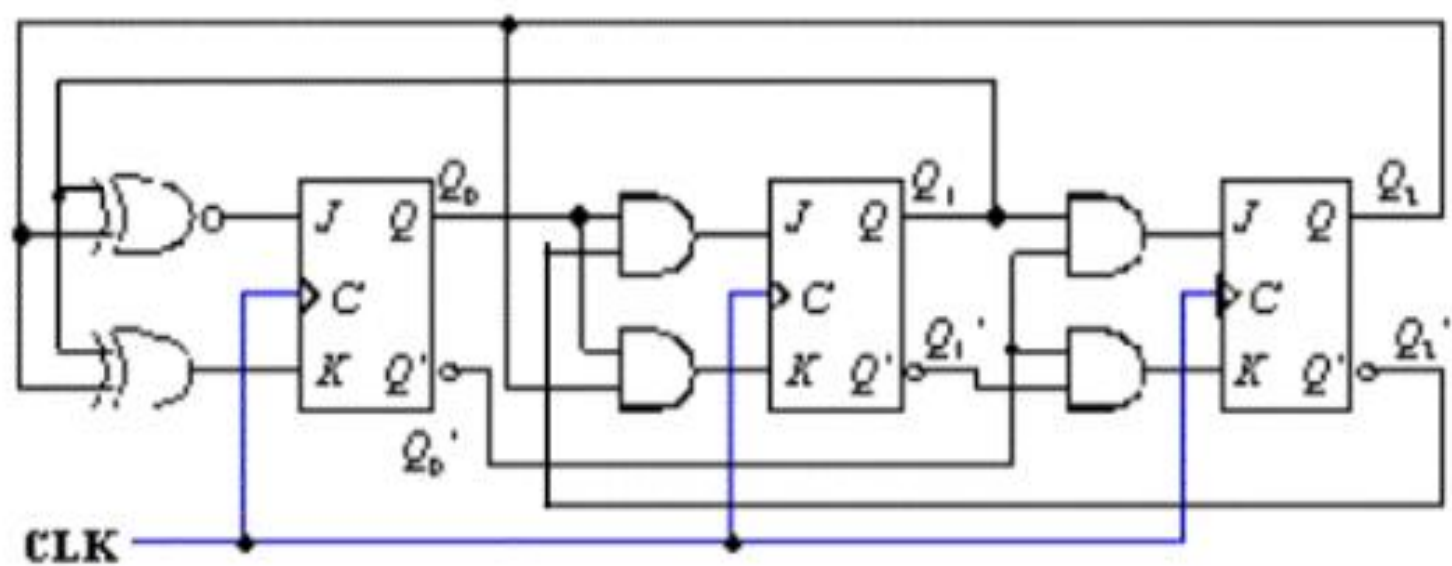

Example 1

- Design a 3 bit synchronous counter using JK flip flops

Example 2

- Design a 3 bit UP/DOWN
[bidirectional]counter using JK Flip flops

Design of synchronous counter with unused states

- **Self starting counter**
 - Whenever a counter goes to an invalid state, it comes back to a valid state in 1 or 2 clock pulses and then starts counting in a normal sequence, it is called self starting.
- **Lock out condition**
 - If a counter enters an invalid state, it keeps on moving from one invalid state to another when clock pulses are applied.
 - It never returns to a valid state.

Example 1

- Design a mod 6 synchronous counter using JK flip flops Check whether the counter is self starting.

Example 2

- Design a synchronous BCD counter using JK flip flops. Check whether the counter is self starting.

Example 3

- Design a synchronous counter using T flip flops that goes through states 0,3,5,6,0..
Check whether the counter is self starting.
Check whether any lock out condition arises.

Design of Asynchronous Counter


Asynchronous Counter

- Can be designed using T or JK flip flops
- These flip flops are used in toggle mode
- The flip flops are not clocked simultaneously
- The out put of previous flip flop becomes input to the next flip flop, hence asynchronous.
- The inputs J and K of the flip flops are 1, this acts as a toggle switch and out put of flip flop is complemented.

Mod M Asynchronous Counter

- An n bit asynchronous counter counts $N = 2^n$ clock pulses.
- To count M clock pulses, which is less than N, the Reset terminal of Flip flop is used.
- A combinational circuit is designed such that all the flip flops are reset after the count M.
- The out put of the combinational circuit must be zero after M clock pulses

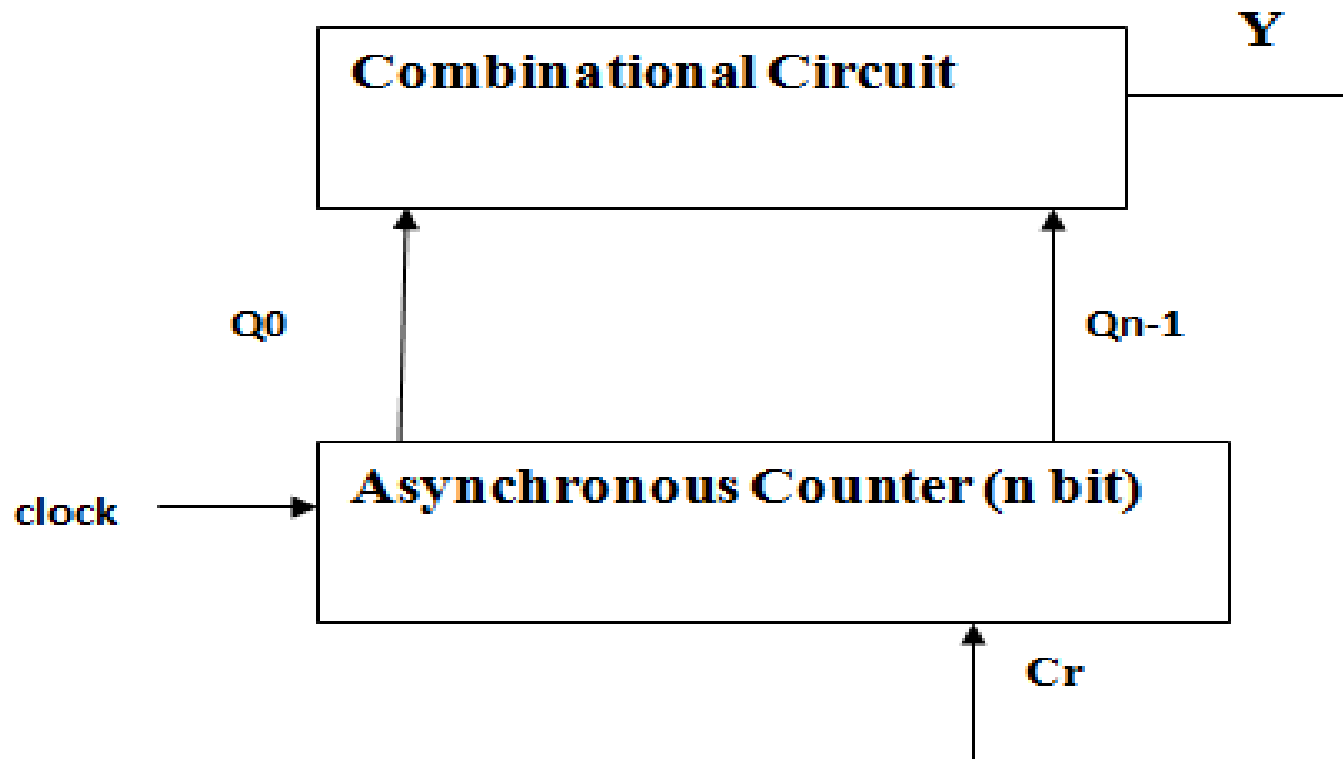Block diagram of Mod M asynchronous counter



Procedure to design a Mod M Asynchronous Counter

- Find the minimum number of flip flops required($n: M < 2^n$).
- Prepare the sequence.
- Design the combinational circuit such that all the flip flops are reset after M clock pulses.
 - Draw the truth table of the asynchronous counter with out put of the combinational circuit (Y) such that Y=1 for valid states and Y=0 for invalid states
 - Find out simplified expression for Y using K map
 - Draw the logic diagram

Example 1

- Design a Mod 4 ripple counter using JK flip flops.

Example 2

- Design a Mod 9 ripple counter using T flip flops.

Synthesis of synchronous Sequential Circuits



Synthesis of synchronous Sequential Circuits

- Steps are
 - Form a description of the problem through a state table/diagram.
 - If possible, reduce states.
 - Make state assignment and derive the transition or out put table
 - Select the type and number of memory elements to be used
 - Using k map, obtain minimal expression for the flip flop inputs
 - Draw the logic diagram

Synthesis of synchronous Sequential Circuits

- Serial binary adder
- Sequence generator
- Sequence detector


Serial binary adder

  

Sequence Generator

- This is a sequential circuit which generates a desired sequence of bits in synchronisation with a clock.
- Also called pulse generator, in which a particular repetitive series of pulses are generated

Block Diagram

 

To design a sequence generator,

- first calculate the number of flip flops required
- Then, design the next state decoder to generate the desired sequence

Design procedure

1) Find the minimum number of flip flops required (n).

- It depends on the nature of sequence
- Can be calculated using the equation

$$\text{Max}(C_0, C_1) \leq 2^{n-1}$$

Here, C_0 is the count of zeros and C_1 is the count of ones.

2) Draw the state table as per the following procedure

- Starting from LSB, assign the desired sequence to the out put of the flip flops, which produces the out put
- Assign the out put of the other flip flops 0 or 1, such that all the states are different.

- 3) Draw the state diagram
- 4) Compute the inputs to the flip flops and simplify
- 5) Draw the logic diagram

Example 1

- Design a sequence generator using D flip flops to generate the sequence 101100110

Sequence Detector

- It is a sequential machine which produces an out put of 1 every time the desired sequence is detected, otherwise, gives output as 0.

Example 1

- Design a sequence detector to detect the sequence 1010 and overlapping is permitted. Assume the input sequence is 01101010 and the corresponding output sequence is 00000101