







Boolean Algebra and Digital Logic

Basic Logic Block-Gates

Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
I		$X = A'$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
NAND		$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																

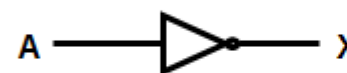XOR
Exclusive OR



$$X = A \oplus B$$

or

$$X = A'B + AB'$$

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

XNOR
Exclusive NOR
or Equivalence



$$X = (A \oplus B)'$$

or

$$X = A'B' + AB$$

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

Boolean Algebra

- Boolean algebra is a mathematical system for the manipulation of variables that can have one of two values.
 - In formal logic, these values are “true” and “false.”
 - In digital systems, these values are “on” and “off,” 1 and 0, or “high” and “low.”
- Boolean expressions are created by performing operations on Boolean variables.
 - Common Boolean operators include AND, OR, and NOT.

- A Boolean operator can be completely described using a truth table.
- The AND operator is also known as a Boolean product.
- The OR operator is the Boolean sum.

- A Boolean function has:
 - At least one Boolean variable,
 - At least one Boolean operator, and
 - At least one input from the set $\{0,1\}$.
- It produces an output that is also a member of the set $\{0,1\}$.

- A *Boolean algebra* is defined as a closed algebraic system containing a set K or two or more elements and the two operators, . and +.
- Useful for identifying and *minimizing* circuit functionality
- Identity elements
 - $a + 0 = a$
 - $a . 1 = a$
 - 0 is the identity element for the + operation.
 - 1 is the identity element for the . operation.

Commutativity and Associativity of the Operators

- The Commutative Property:

$$a + b = b + a$$

$$a \cdot b = b \cdot a$$

- The Associative Property:

$$a + (b + c) = (a + b) + c$$

$$a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

- The Distributive Property:

$$a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

- The Existence of the Complement:

For every a there exists a unique element called a' (*complement of a*) such that,

$$a + a' = 1$$

$$a \cdot a' = 0$$

- To simplify notation, the . operator is frequently omitted. When two elements are written next to each other, the AND (.) operator is implied

$$a + b . c = (a + b) . (a + c)$$

$$a + bc = (a + b)(a + c)$$

Duality

- The principle of *duality* says that if an expression is valid in Boolean algebra, the dual of that expression is also valid.
- To form the dual of an expression, replace all + operators with . operators, all . operators with + operators
- Form the dual of the expression $F = a + (bc)$
Dual of F is $(a + b)(a + c)$

Involution

- Taking the double inverse of a value will give the initial value.

Absorption

- This theorem states:

$$a + ab = a$$

$$a(a+b) = a$$

- To prove the first half of this theorem:

$$a + ab = a \cdot 1 + ab$$

$$= a (1 + b)$$

$$= a (b + 1)$$

$$= a (1)$$

$$a + ab = a$$

DeMorgan's Theorem

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$

- Find the complement of:

$$F = (AB' + C)D' + E$$

$$F' = [(AB' + C)D' + E]'$$

$$= [(AB' + C)D']' E'$$

$$= [(AB' + C)' + D''] E'$$


$$= [(AB')' C' + D] E'$$

$$= (A' + B) C' E' + DE'$$

Boolean Functions

- Boolean algebra deals with binary variables and logic operations.
- Function results in binary 0 or 1

x	y	z	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

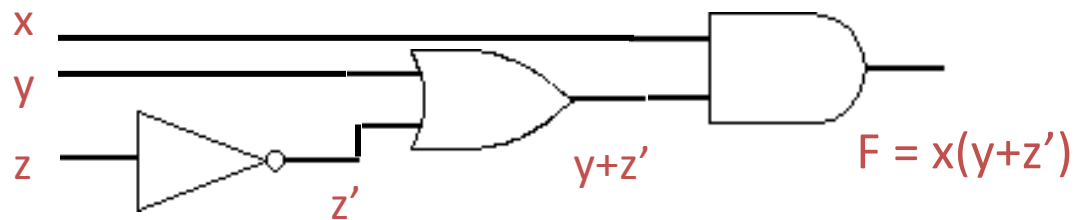

$$F = x(y + z')$$

Simplifying Boolean Functions

- Simplify the following Boolean function to a minimum number of terms: $F = xy + x'z + yz$

$$\begin{aligned}F_3 &= xy + x'z + yz \\&= xy + x'z + yz(x + x') \\&= xy + x'z + xyz + x'yz \\&= xy(1 + z) + x'z(1 + y) \\&= xy + x'z\end{aligned}$$

- ***Any Boolean Expression can be represented in two forms:***
 - *sum of products (SOP)*
 - *Product of Sum (POS)*

SOP Form

- Each variable in a Boolean expression is a **literal**
- Boolean variables can appear in normal (x) or complement form (x')
- Each AND combination of terms is a minterm

Minterms

x	y	z	Minterm	
0	0	0	$x'y'z'$	m_0
0	0	1	$x'y'z$	m_1
...				
1	0	0	$xy'z'$	m_4
...				
1	1	1	xyz	m_7

POS form

- Each OR combination of terms is a maxterm

Maxterms

x	y	z	Maxterm	
0	0	0	$x+y+z$	M_0
0	0	1	$x+y+z'$	M_1
...				
1	0	0	$x'+y+z$	M_4
...				
1	1	1	$x'+y'+z'$	M_7

- Note that each maxterm is the complement of its corresponding minterm and vice versa.

Minterms and Maxterms for Three Binary Variables

x	y	z	minterms		Maxterms	
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_5	$x'+y+z'$	M_5
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

Given the truth table, express F_1 in sum of minterms

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned} F_1(x, y, z) &= \sum(1, 4, 5, 6, 7) = m_1 + m_4 + m_5 + m_6 + m_7 \\ &= (x' y' z) + (x y' z') + (x y' z) + (x y z') + (x y z) \end{aligned}$$

- For product of maxterms:

x	y	z	F_1	F_2
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F_1(x, y, z) = \Pi(0,2,3) = M_0 \cdot M_2 \cdot M_3$$

$$= (x + y + z)(x + y' + z)(x + y' + z')$$

Minimization with Karnaugh Maps

Gate-Level Minimization

- The Boolean functions also can be simplified by map method as **Karnaugh map** or **K-map**.
- The map is made up of squares, with **each square** representing **one minterm** of the function.
- This produces a circuit diagram with a minimum number of gates and the minimum number of inputs to the gate.
- It is sometimes possible to find two or more expressions that satisfy the minimization criteria.


- A Kmap is a matrix consisting of rows and columns that represent the output values of a Boolean function.
- The output values placed in each cell are derived from the minterms of a Boolean function.
- A *minterm* is a product term that contains all of the function's variables exactly once, either complemented or not complemented.

- K-maps are often used to simplify logic problems with 2, 3 or 4 variables.
- **Cell = 2^n ,where n is a number of variables**

Two-Variable K map

- A two-variable function has four possible minterms. We can re-arrange these minterms into a **Karnaugh map (K-map)**.

x	y	minterm
0	0	$x'y'$
0	1	$x'y$
1	0	xy'
1	1	xy

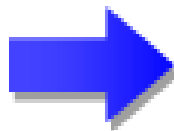

		y	
		0	1
x	0	$x'y'$	$x'y$
	1	xy'	xy

m_0	m_1
m_2	m_3

		y		
		$x \swarrow$		
			$\overbrace{\hspace{1.5cm}}$	
			$0 \qquad 1$	
x	$\left\{ \begin{array}{l} 0 \\ 1 \end{array} \right.$	0	$x'y'$	$x'y$
		1	xy'	xy

- For the Boolean expression


$m_1 + m_2 + m_3 = x'y + xy' + xy$, 2 variable K map is

		y	
		0	1
x	0		1
	1	1	1

Three-Variable K map

- For a three-variable expression with inputs x , y , z , the arrangement of minterms follows Gray code.
- For simplifying Boolean functions, we must recognize the basic property possessed by adjacent squares.
- Each cell differs from an adjacent cell by only one variable

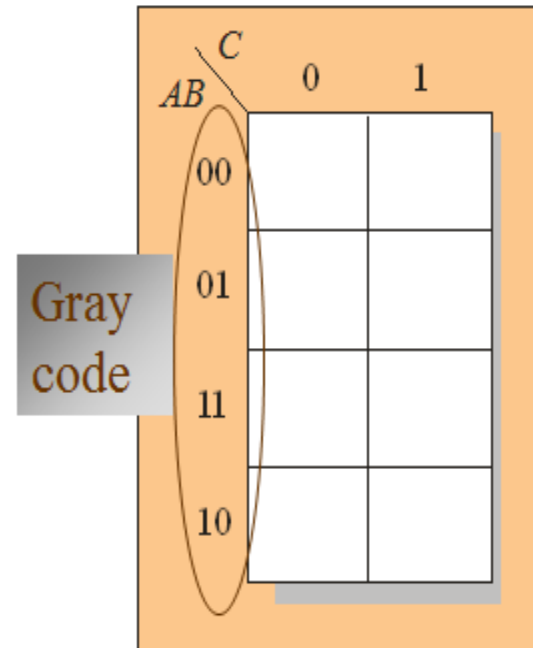- Cells are usually labeled using 0's and 1's to represent the variable and its complement
- The numbers are entered in gray code, to force adjacent cells to be different by only one variable.
- Ones are read as the true variable and zeros are read as the complemented variable.



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	1	1	1

$$F = AB'C' + AB'C + ABC + ABC' + A'B'C + A'BC'$$

- Minterms which are identical, except for one variable, are considered to be adjacent to one another.
- $m_5 + m_7 = xy'z + xyz = xz(y' + y) = xz$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		y					
		z		00	01	11	10
x	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$		
	1	$xy'z'$	$xy'z$	xyz	xyz'		
y		z					

- With this ordering, any group of 2, 4 or 8 adjacent squares on the map contains common literals that can be factored out.

				y
	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
x	$xy'z'$	$xy'z$	xyz	xyz'
				z

$$\begin{aligned}
 & x'y'z' + xy'z' + x'yz' + xyz' \\
 &= z'(x'y' + xy' + x'y + xy) \\
 &= z'(y'(x' + x) + y(x' + x)) \\
 &= z'(y' + y) \\
 &= z'
 \end{aligned}$$

Four-variable K map

Can accommodate 16 minterms that are produced by a four-input function.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

		yz		y	
		0 0	0 1	1 1	1 0
w	wx				
	0 0	$w'x'y'z'$	$w'x'y'z$	$w'x'yz$	$w'x'yz'$
	0 1	$w'xy'z'$	$w'xy'z$	$w'xyz$	$w'xyz'$
	1 1	$wxy'z'$	$wxy'z$	$wxyz$	$wxyz'$
	1 0	$wx'y'z'$	$wx'y'z$	$wx'yz$	$wx'yz'$
		z			

x

- $F = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$

The function can be written as:

$$F = A'B'C'D' + A'B'CD' + A'B'CD + A'BC'D + A'BCD' + A'BCD + AB'C'D' + AB'CD' + AB'CD + ABCD' + ABCD$$

AB \ CD		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	0	0	1	1
	10	1	0	1	1

Insert 1 in those cells where the function F has a value of 1. Put 0 in the other cells.

Simplification using 2 variable K map

- Is done by finding adjacent 1s in the Kmap that can be collected into groups that are powers of two.

- The rules of Kmap simplification are:
 - Groupings can contain only 1s; no 0s.
 - Groups can be formed only at right angles; diagonal groups are not allowed.
 - The number of 1s in a group must be a power of 2 – even if it contains a single 1.
 - The groups must be made as large as possible.
 - Groups can overlap and wrap around the sides of the Kmap.

		Y	
		0	1
X	0	0	1
	1	1	1

Simplification using 3 variable K map

$$F(X, Y, Z) = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z}$$

X \ YZ	YZ			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

X \ YZ	YZ			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

reduced function is

$$F(X, Y, Z) = \bar{X} + \bar{Z}$$

$$F = AB'C' + AB'C + ABC + ABC' + A'B'C + A'BC'$$


		BC			
		00	01	11	10
A	0	0	1	0	1
	1	1	1	1	1

$$F = A + B'C + BC'$$

Simplification using 4 variable K map

$$F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}Y\bar{Z} + \bar{W}XY\bar{Z} + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}\bar{Y}Z + W\bar{X}Y\bar{Z} + WXY\bar{Z}$$

WX \ YZ	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

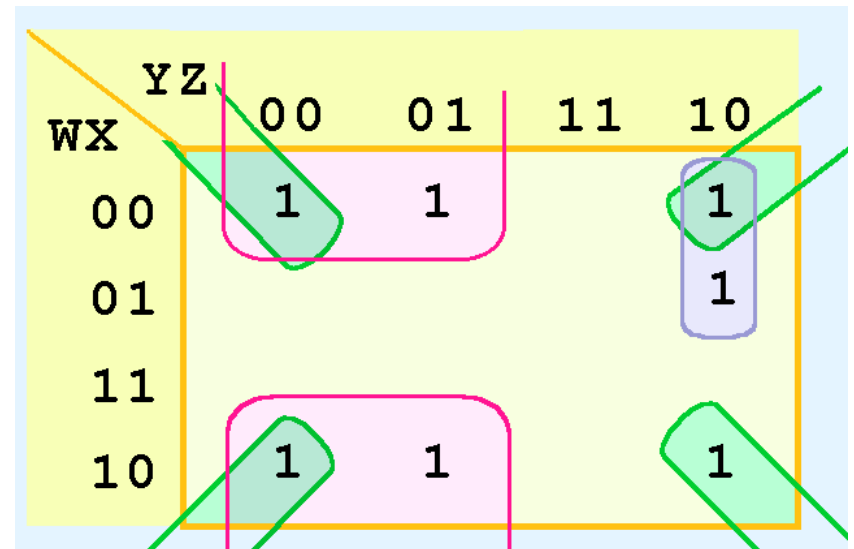

$$F(W, X, Y, Z) = \bar{W}\bar{Y} + \bar{X}\bar{Z} + \bar{W}Y\bar{Z}$$

Don't Care Conditions

- Real circuits don't always need to have an output defined for every possible input.
- If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a *don't care* condition.
- In a Kmap, a don't care condition is identified by an **X** in the cell of the minterm(s) for the don't care inputs
- In performing the simplification, we are free to include or ignore the *X*'s when creating our groups.

Karnaugh maps: Don't cares

- $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	X
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	X
1	1	0	1	X
1	1	1	0	0
1	1	1	1	0

- In some situations, we don't care about the value of a function for certain combinations of the variables.
 - these combinations may be impossible in certain contexts
 - or the value of the function may not matter in when the combinations occur

Map Simplification with Don't Cares

$AB \backslash CD$		CD			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$$F = A'C'D + B + AC$$

Alternative covering.

$AB \backslash CD$		CD			
		00	01	11	10
00	00	0	1	0	0
01	01	x	x	x	1
11	11	1	1	1	x
10	10	x	0	1	1

$$F = A'B'C'D + ABC' + BC + AC$$

Example

- Use a K-Map to simplify the following Boolean expression

$$F(a,b,c,d) = \sum m(0,2,6,8,12,13,15) + d(3,4,9)$$

$$F(a,b,c,d) = \sum m(0,2,6,8,12,13,15) + d(3,4,9)$$

ab \ cd		00	01	11	10
cd	00	1	d	1	1
	01			1	d
	11	d		1	
	10	1	1		

		ab			
		00	01	11	10
cd	00	1	d	1	1
	01			1	d
	11	d		1	
	10	1	1		

$$F = a\bar{c} + \bar{a}\bar{d} + abd$$

Universal Logic Gates

- NAND
- NOR




The NAND Gate

- Therefore, we can use a NAND gate to implement all three of the *elementary operators* (AND,OR,NOT).
- Therefore, ANY switching function can be constructed using only NAND gates. Such a gate is said to be *primitive* or *functionally complete*.



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gates into Other Gates

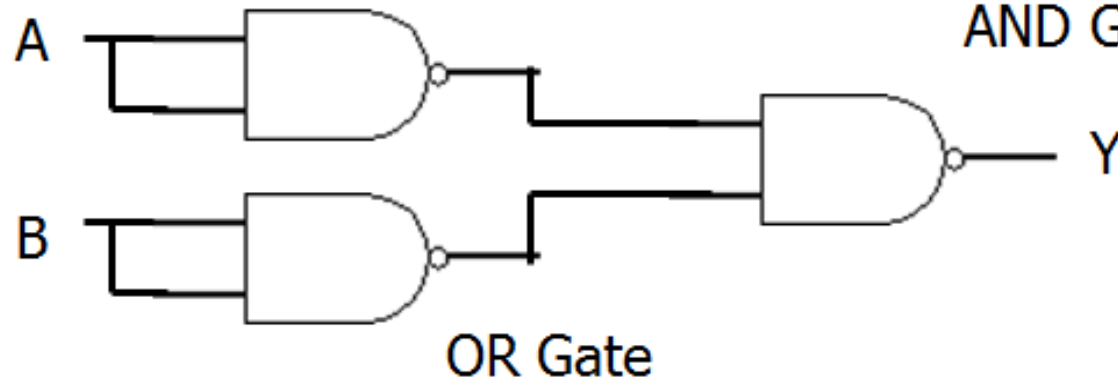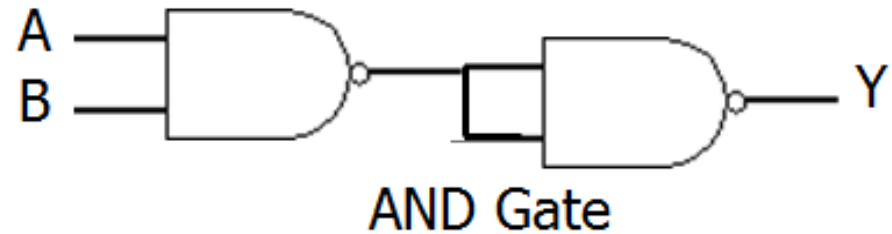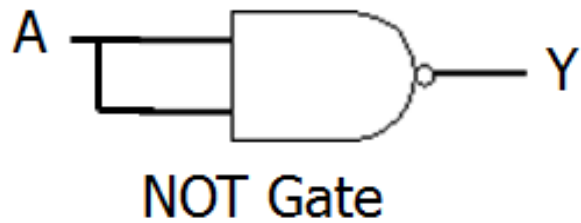




The NOR Gate

- Just like the NAND gate, the NOR gate is functionally complete, ie, any logic function can be implemented using just NOR gates.




A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


NOR Gates into Other Gates

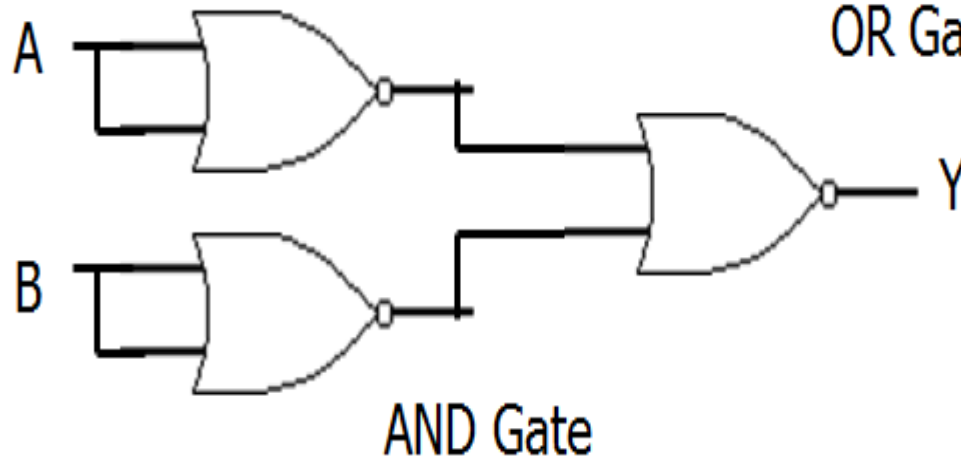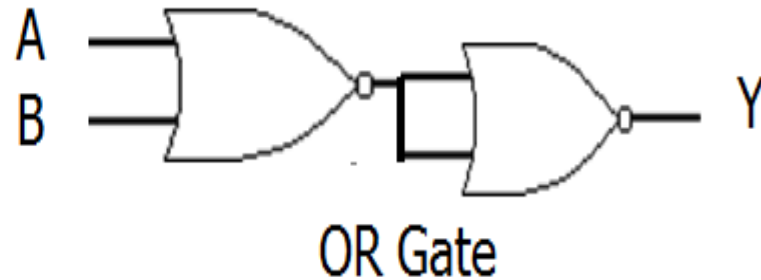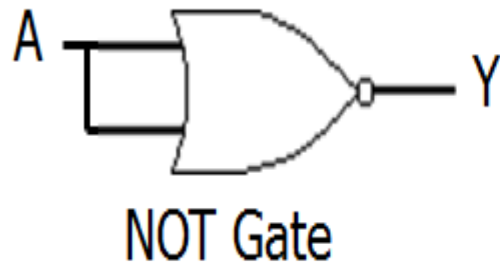


Universality of NAND gates

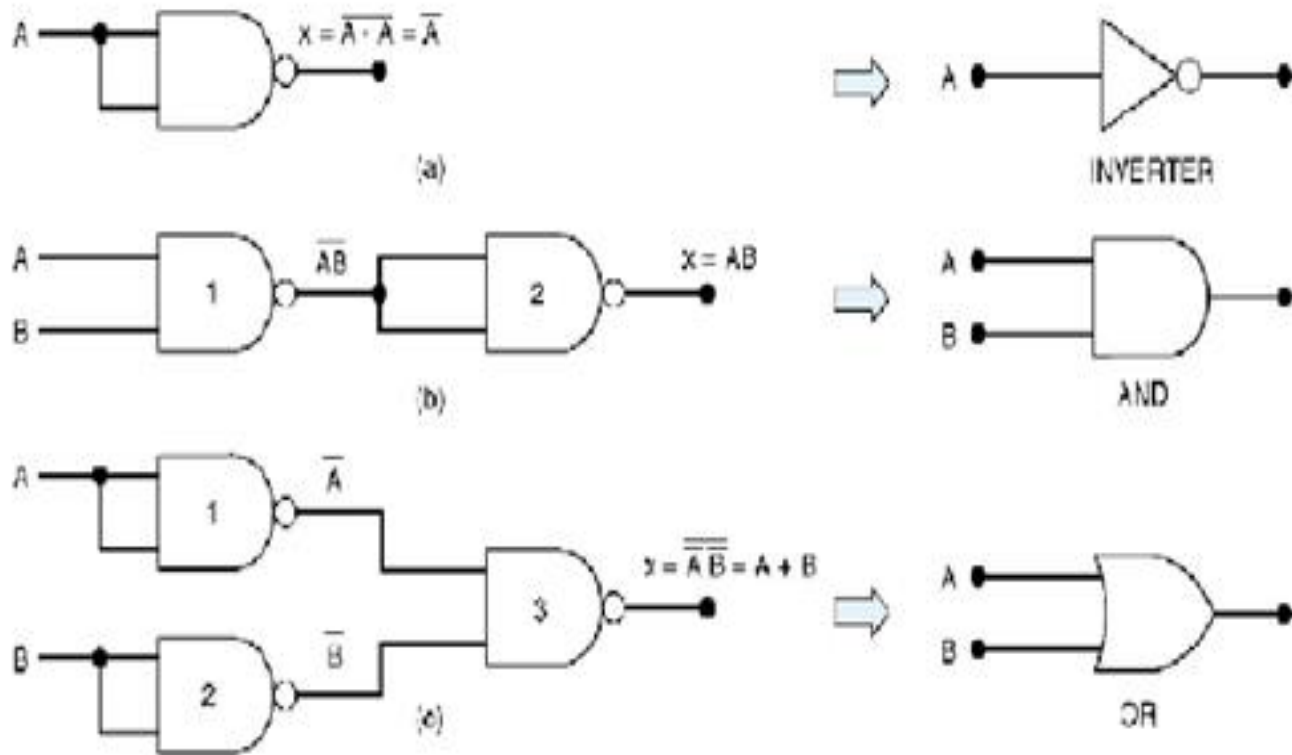


Universality of NOR gate

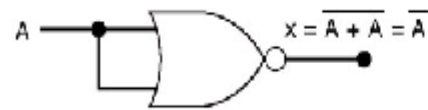

(a)

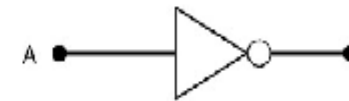


INVERTER

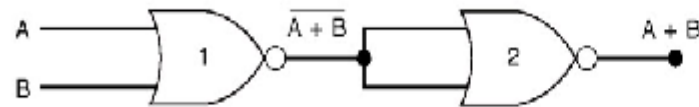


(b)



OR

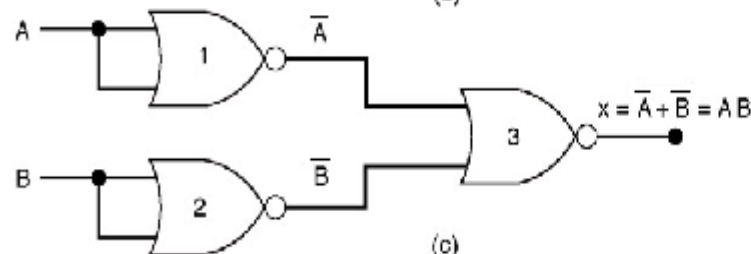

(c)

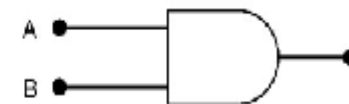

AND

- Boolean algebra defines how binary variables with NAND, NOR can be combined
- DeMorgan's rules are important.
 - Allow conversion to NAND/NOR representations