

# Control Design: Hardwired Approach

Bidyut Kr. Patra

Book: P.Hayes. Computer Architecture and Organization, McGraw-Hill

# Control Design: Hardwired Approach



## Control Design: Hardwired Approach

- **Method 1:** Classical Method of sequential circuit design. (Optimized in terms of Flip-flop (FF) requirement)
- **Method 2:** One hot method. (Simple circuit)

## Classical Method:GCD Processor

- Design a control unit for GCD processor using Classical method.

## GCD Processor

### Procedure for computing GCD in HDL

gcd(in:X, Y;out:Z)

- ① register  $XR$ ,  $YR$ ,  $TEMPR$ ;
- ②  $XR := X$ ;  $YR := Y$ ; {Input the data}
- ③ while( $XR > 0$ ) do begin
  - if ( $XR \leq YR$ ) then begin
    - ①  $TEMPR := YR$ ;
    - ②  $YR := XR$ ;
    - ③  $XR := TEMPR$ ; { Swap  $XR$  and  $YR$ }
  - ④  $XR := XR - YR$ ; {Subtract}

$Z := YR$  {Output the result}

end gcd;

## Example


$$X = 20, Y = 12$$

Conditions	Actions
$XR > 0 : \quad XR > YR :$	$XR := 20; YR = 12;$
$XR > 0 : \quad XR \leq YR :$	$XR := XR - YR = 8;$
$XR > 0 : \quad XR \leq YR :$	$XR := 12; YR = 8; \quad ;XR = XR - YR = 4;$
$XR > 0 : \quad XR \leq YR :$	$XR := 8; YR = 4; \quad ;XR = XR - YR = 4;$
$XR > 0 : \quad XR \leq YR :$	$XR := 4; YR = 4; \quad ;XR = XR - YR = 0;$
$XR \leq 0$	$Z = 4$

Table: Example

$$\underline{GCD(20, 12) = 4.}$$

## Hardware for GCD Processor

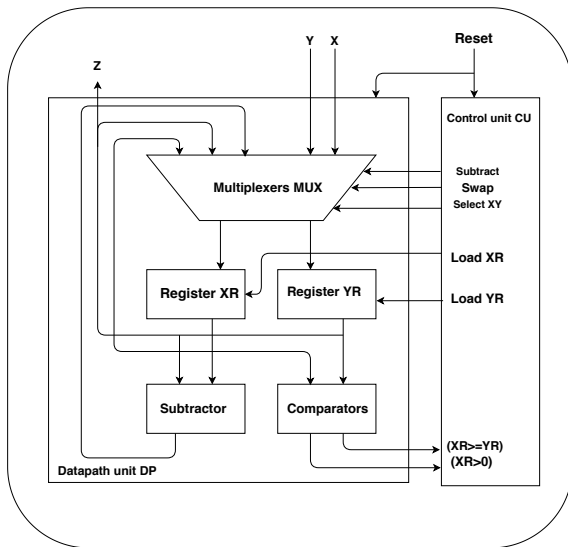



## State Table for Control Unit of GCD Processor

Design the State Table defining the Control Unit of the GCD Processor.

## GCD Processor

### Procedure for computing GCD in HDL

gcd(in:X, Y;out:Z)

- ① register  $XR, YR, TEMPR$ ;
- ②  $XR := X; YR := Y; \{ \text{Input the data: } S_0 \}$
- ③ while( $XR > 0$ ) do begin
  - if ( $XR \leq YR$ ) then begin
    - ①  $TEMPR := YR$ ;
    - ②  $YR := XR$ ;
    - ③  $XR := TEMPR$ ; { Swap  $XR$  and  $YR$ :  $S_1$  }
  - ④  $XR := XR - YR$ ; { Subtract:  $S_2$  }

$Z := YR \{ \text{Output the result: } S_3 \}$

end gcd;

# State Table

Table: State Table of Control Unit (GCD Processor)

State	Inputs $XR > 0$ $XR \geq YR$			Outputs				
	0-	10	11	Subtract	Swap	SelectXY	LoadXR	LoadYR
$S_0$	$S_3$	$S_1$	$S_2$	0	0	1	1	1
$S_1$	$S_2$	$S_2$	$S_2$	0	1	0	1	1
$S_2$	$S_3$	$S_1$	$S_2$	1	0	0	1	0
$S_3$	$S_3$	$S_3$	$S_3$	0	0	0	0	0

## Steps of Classical Design Method

- 1 Construct a P-row state table that defines the desired input-output behaviour.
- 2 Select minimum number  $p$  of D-type flip-flops and assign  $p$ -bit binary code to each state.  $\{S_0 : 00, S_1 : 01, S_2 : 10, S_3 : 11\}$
- 3 Design a combinational circuit  $C$  that generate the primary output signal  $\{z_i\}$  and secondary outputs  $\{D_i\}$  that must be applied to the FFs.

Table: Excitation Table for the control unit of GCD Processor

Inputs		PS		NS		Outputs				
$XR > 0$	$(XR \geq YR)$	$D_1$	$D_0$	$D_1^+$	$D_0^+$	Sub	Sw	XY	XR	YR
0	d	0	0	1	1	0	0	1	1	1
0	d	0	1	1	0	0	1	0	1	1
0	d	1	0	1	1	1	0	0	1	0
0	d	1	1	1	1	0	0	0	0	0
1	0	0	0	0	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0	1	1
1	0	1	0	0	1	1	0	0	1	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	1	1	1
1	1	0	1	1	0	0	1	0	1	1
1	1	1	0	1	0	1	0	0	1	0
1	1	1	1	1	1	0	0	0	0	0

## Steps of Classical Design Method

- 1 Construct a P-row state table that defines the desired input-output behaviour. ✓
- 2 Select minimum number  $p$  of D-type flip-flops and assign  $p$ -bit binary code to each state. ✓
- 3 Design a combinational circuit  $C$  that generate the primary output signal  $\{z_i\}$  and secondary outputs  $\{D_i\}$  that must be applied to the FFs.

Table: Excitation Table for the control unit of GCD Processor

Inputs		PS		NS		Outputs				
$XR > 0$	$(XR \geq YR)$	$D_1$	$D_0$	$D_1^+$	$D_0^+$	Sub	Sw	XY	XR	YR
0	d	0	0	1	1	0	0	1	1	1
0	d	0	1	1	0	0	1	0	1	1
0	d	1	0	1	1	1	0	0	1	0
0	d	1	1	1	1	0	0	0	0	0
1	0	0	0	0	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0	1	1
1	0	1	0	0	1	1	0	0	1	0
1	0	1	1	1	1	0	0	0	0	0
1	1	0	0	1	0	0	0	1	1	1
1	1	0	1	1	0	0	1	0	1	1
1	1	1	0	1	0	1	0	0	1	0
1	1	1	1	1	1	0	0	0	0	0

Classical Method: $D_1^+$ :

Truth table for  $D_1^+$  based on  $D_0$  and  $(X, Y)$  comparisons:


$D_1 D_0$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10		1	1	

Annotations from the diagram:

- Top-left:  $(\overline{X}R > 0)$  and  $(\overline{X}R > YR)$
- Top-right:  $(\overline{X}R > 0)$
- Middle-right:  $(\overline{X}R > YR)$
- Bottom-right:  $(\overline{X}R > 0)$  and  $(\overline{X}R > YR)$
 
$$D_1^+ = D_0 + (X \gg Y) + (\overline{X}R > 0)$$





$$D_0^+ = D_0 D_1 + \bar{D}_0 \cdot (X_R > 0) + \bar{D}_0 \cdot (X_R > 0) \cdot (X_R \geq Y_R) + (X_R \geq Y_R) \cdot \bar{D}_0$$

$$\text{Subtract} = \bar{D}_0 \cdot D_1$$

$$\text{Swap} = \bar{D}_1 \cdot D_0$$

$$\text{Select } \times Y = \bar{D}_0 \cdot \bar{D}_1$$

$$\begin{aligned} \text{Load } \times R &= \bar{D}_1 \bar{D}_0 + \bar{D}_1 D_0 + \bar{D}_1 \bar{D}_0 \\ &= \bar{D}_0 (\bar{D}_1 + D_1) + \bar{D}_1 \cdot D_0 \\ &= \bar{D}_0 + \bar{D}_1 \cdot D_0 \\ &= (\bar{D}_0 + \bar{D}_1) \cdot (\bar{D}_0 + D_0) \\ &= \bar{D}_0 + \bar{D}_1 \end{aligned}$$

$$\text{Load } \times R = \bar{D}_1$$

## Step 3: Generate output signals

$$D_1^+ = \overline{XR > 0} + (XR \geq YR) + D_0$$

$$D_0^+ = D_1 \cdot D_0 + \overline{(XR \geq XY)} \cdot \bar{D}_0 + \overline{(XR > 0)} \cdot \bar{D}_0$$

$$\text{Subtract} = D_1 \cdot \bar{D}_0$$


$$\text{Swap} = \bar{D}_1 \cdot D_0$$

$$\text{SelectXY} = \bar{D}_1 \cdot \bar{D}_0$$

$$\text{LoadXR} = \bar{D}_0 + \bar{D}_1$$

$$\text{LoadYR} = \bar{D}_1$$

**Table:** Outputs of the Control ckt.

 

Scanned with CamScanner

Figure:

## One-hot Method

- 1 No need to have excitation table for designing the circuit. The  $P$ -row state table is sufficient.
- 2 Associate a separate D-type flip-flop  $D_i$  with each state  $S_i$ , and assign the  $P$ -bit one-hot binary code  
 $D_1, D_2, \dots, D_i, D_{i+1}, \dots, D_P = 00 \dots 10 \dots 0$
- 3 Design a combinational circuit  $C$  that generates the primary and secondary output signals  $\{z_i\}$  and  $\{D_i\}$ , respectively.

## Designing the Combinational Circuit from State Table

- $D_i^+ = \sum_i^P D_i(I_{j,1} + I_{j,2} + \dots + I_{j,n_j})$   
 where,  $I_{j,1} + I_{j,2} + \dots + I_{j,n_j}$  are the all input combinations that cause a transition from  $S_j$  to  $S_i$ .  
 Identify all transitions ( $PS \rightarrow NS$ ) involving next state as  $S_i$ .
- $z_k = D_{k,1} + D_{k,2} \dots + D_{k,m_h}$   
 Identify the present states for which  $z_k = 1$ , then take combination of all those present states (ORing)

# State Table

Table: State Table of Control Unit (GCD Processor)

State	Inputs $XR > 0$ $XR \geq YR$			Outputs				
	0-	10	11	Subtract	Swap	SelectXY	LoadXR	LoadYR
$S_0$	$S_3$	$S_1$	$S_2$	0	0	1	1	1
$S_1$	$S_2$	$S_2$	$S_2$	0	1	0	1	1
$S_2$	$S_3$	$S_1$	$S_2$	1	0	0	1	0
$S_3$	$S_3$	$S_3$	$S_3$	0	0	0	0	0

$S_0$  : 0001;  $S_1$  : 0010;  $S_2$  : 0100;  $S_3$  : 1000

## Design the circuit

- ①  $\rightarrow S_0 : D_0^+ = 0$
- ②  $\rightarrow S_1 : S_0 \rightarrow S_1; \quad \overline{S_2 \rightarrow S_1}$   
 $D_1^+ = D_0.(XR > 0)(\overline{XR \geq YR}) + D_2.(XR > 0)(\overline{XR \geq YR})$
- ③  $\rightarrow S_2 : S_0 \rightarrow S_2(11); S_1 \rightarrow S_2(0-, 10, 11); S_2 \rightarrow S_2(11)$   
 $D_1^+ = D_1 + D_2.(XR > 0).(XR \geq XY) + D_0.(XR > 0).(XR \geq XY)$
- ④  $\rightarrow S_3 : S_0 \rightarrow S_3(0-); S_2 \rightarrow S_3(0-); S_3 \rightarrow S_3(0-, 10, 11)$   
 $D_3^+ = D_3 + D_2.(XR > 0) + D_0.(XR > 0)$



# State Table

Table: State Table of Control Unit (GCD Processor)

State	Inputs $XR > 0$ $XR \geq YR$			Outputs				
	0-	10	11	Subtract	Swap	SelectXY	LoadXR	LoadYR
$S_0$	$S_3$	$S_1$	$S_2$	0	0	1	1	1
$S_1$	$S_2$	$S_2$	$S_2$	0	1	0	1	1
$S_2$	$S_3$	$S_1$	$S_2$	1	0	0	1	0
$S_3$	$S_3$	$S_3$	$S_3$	0	0	0	0	0

$S_0$  : 0001;  $S_1$  : 0010;  $S_2$  : 0100;  $S_3$  : 1000

## Primary Signals

- ➊ Subtract= $D_2$
- ➋ Swap= $D_1$
- ➌ Select XY= $D_0$
- ➍ Load XR= $D_0 + D_1 + D_2$
- ➎ Load YR= $D_0 + D_1$

THANK YOU